

University of Moratuwa
Faculty of Engineering
Department of Electronic & Telecommunication
Engineering




EN2111 – Electronic Circuit Design
Project Final Report
Group 13

Group Members	
Index No	Name
220448C	Pathirana P.D.R.O.
220040T	Arachchi M.B.F
220310X	Karunathilake K.D.K.
220449F	Pathirana P.N.A

Table of Contents

1.	Circuit diagram and explanation of circuits.....	3
2.	Calculations of cutoff frequencies.....	5
3.	Simulation bode plots.....	6
4.	Real data plots and MATLAB Plots.....	9
5.	Compare the plots real and simulation.....	12

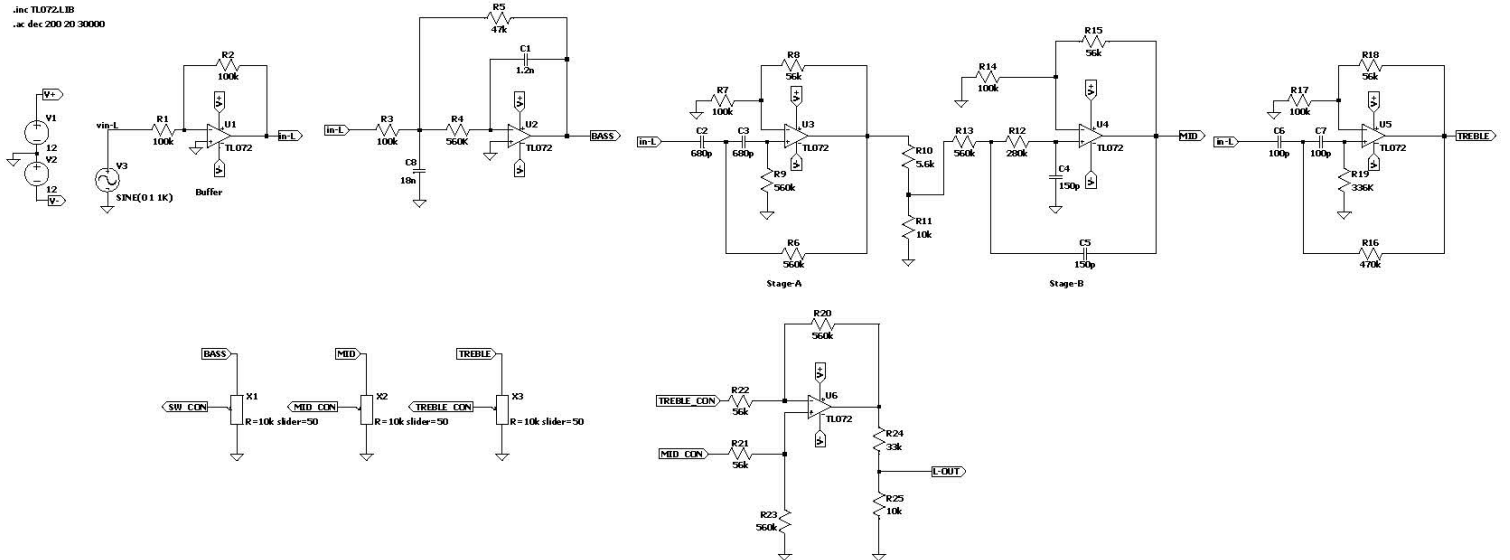1. Circuit diagram and explanation of circuit



This project involves designing and implementing a three-band audio pre-amplifier with split output for subwoofer systems, fulfilling analog design requirements such as filters, feedback, and amplification stages. It serves as a front-end signal conditioner in audio systems, suitable for enhancing sound quality before driving a power amplifier.

1.1 Circuit Working Principle

1.1.1. Amplifier Stages

- The system is divided into two major stages:
 - **Pre-amplifier:** Amplifies low-level signals from sources like mobile or PC and applies equalization.
 - **Power amplifier (external):** Drives loudspeakers with high current/voltage signals.
 -

1.1.2. Input Buffer Stage

- A **unity-gain buffer** (gain ≈ 1 , using TL072 op-amp) is placed at the input.
- It prevents **loading effects** and ensures **impedance matching** with the audio source.

1.1.3. Filter Bank (Equalizer Section)

The incoming signal is split into **three bands** using **active filters**:

A. Low-Pass Filter (Bass/Subwoofer)

- Type: **Multiple Feedback (MFB)** topology
- Cutoff: ~ 250 Hz
- Output goes to both:
 - **Subwoofer amplifier**
 - Combined mix for main output (optional)
- Gain: Configured for ~ 13 dB

B. Mid-Band Filter

- Type: **Band-pass** (Cascaded High-Pass + Low-Pass using Sallen-Key)
 - HPF cutoff: ~ 420 Hz
 - LPF cutoff: ~ 2.3 kHz
- Gain: ~ 1.586 (using damping factor $\zeta = 0.707$ for Butterworth)
- Mid frequencies enhance vocals/instruments.

C. High-Pass Filter (Treble)

- Type: **Sallen-Key**
- Cutoff: ~ 3.3 kHz
- Gain and damping factor tuned for smooth Butterworth response

1.1.4. Tone Control (Potentiometers)

- Each band output is connected to a **potentiometer**:
 - Users can **boost/cut bass, mid, and treble** independently.
- Pot wipers:
 - **Bass** \rightarrow Subwoofer amplifier
 - **Mid & Treble** \rightarrow Summed in an **adder op-amp** \rightarrow Main amplifier

2. Calculations of cutoff frequencies

2.1 Bass

$$\begin{aligned} f_c &= \frac{1}{2\pi\sqrt{R_4 R_5 C_1 C_0}} \\ &= \frac{1}{2\pi\sqrt{(560 \times 10^3)(47 \times 10^3)(1.2 \times 10^{-9})(18 \times 10^{-9})}} \\ &\approx 211.09 \text{ Hz} \end{aligned}$$

This bass stage is a second-order Butterworth low-pass filter in a multiple-feedback topology, with a cutoff frequency of approximately 211.09 Hz, matching the simulation results closely.

2.2 Mid

The mid stage is implemented as 2 stages: stage A and stage B.

Stage A

$$\begin{aligned} f_c &= \frac{1}{2\pi\sqrt{R_6 R_9 C_2 C_3}} \\ &= \frac{1}{2\pi\sqrt{(560 \times 10^3)(560 \times 10^3)(680 \times 10^{-12})^2}} \\ &\approx 418.02 \text{ Hz}, \end{aligned}$$

This stage implements a 2nd-order high-pass multiple-feedback topology, producing a sharp transition from rejection of low frequencies into a flat midband. Its calculated cutoff is 418.02Hz, which aligns closely with the simulated value. As a result, low-frequency signals are effectively removed while the desired midrange passes through unchanged.

Stage B

$$\begin{aligned} f_c &= \frac{1}{2\pi\sqrt{R_{12} R_{13} C_4 C_5}} \\ &= \frac{1}{2\pi\sqrt{(280 \times 10^3)(560 \times 10^3)(150 \times 10^{-12})^2}} \\ &\approx 2677.26 \text{ Hz}. \end{aligned}$$

This stage is the complementary 2nd-order low-pass multiple-feedback section, shaping the upper edge of the mid-band. Its theoretical cutoff is 2677.26Hz, matching closely the simulation's observed value. Below this knee the filter passes the mid-band with unity gain, and above it the response falls away to suppress unwanted high-frequency content.

2.3 Treble

$$f_c = \frac{1}{2\pi\sqrt{R_{16} R_{19} C_6 C_7}}$$


$$= \frac{1}{2\pi\sqrt{(470 \times 10^3)(336 \times 10^3)(100 \times 10^{-12})^2}}$$


$$\approx 4002.62 \text{ Hz.}$$

This stage is a 2nd-order high-pass multiple-feedback filter that defines the treble shelf by sharply passing high-frequency content while attenuating everything below its corner. Its calculated cutoff of approximately 4 kHz closely matches the simulated knee, ensuring that frequencies above this point are boosted or passed through unchanged as intended for clear treble response.



3. Simulation bode plots

Base


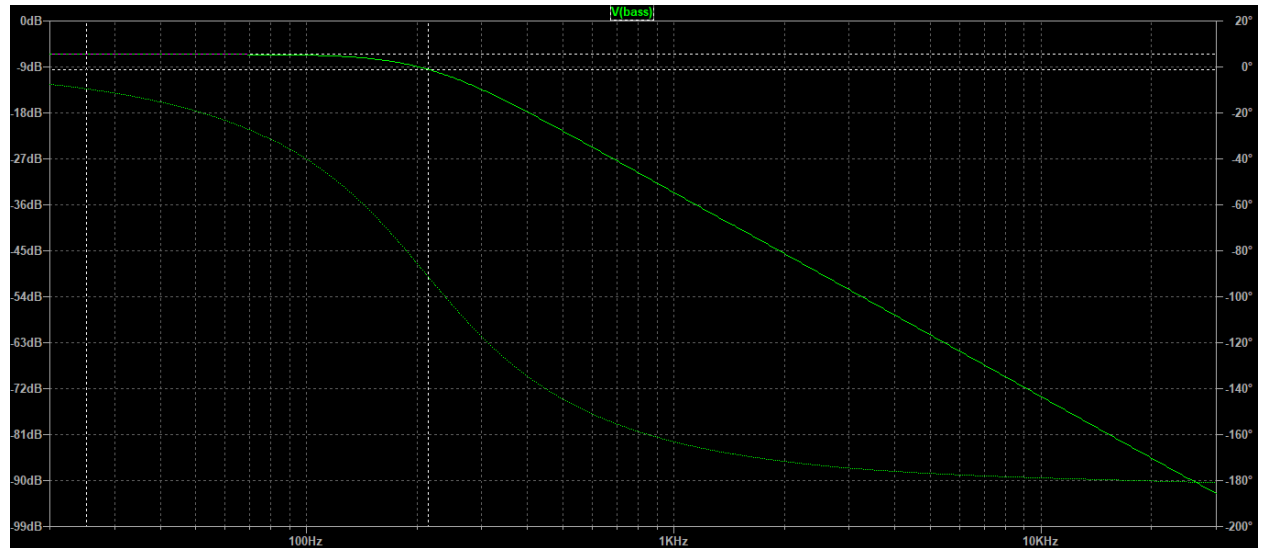


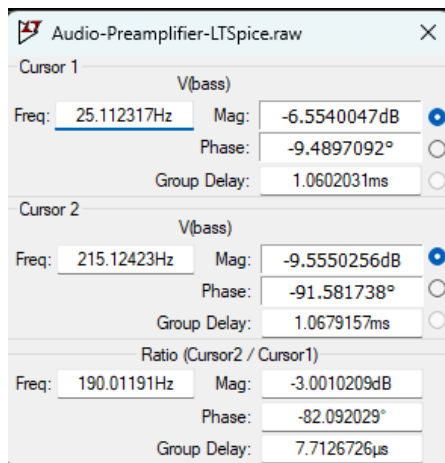

Mid

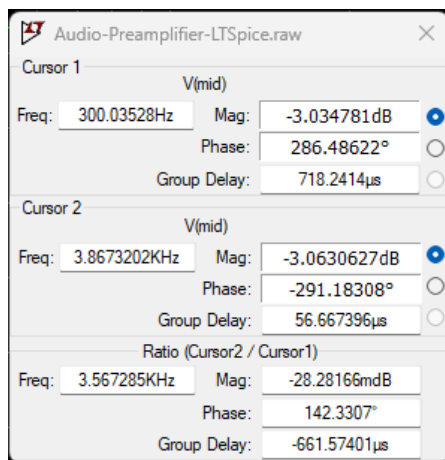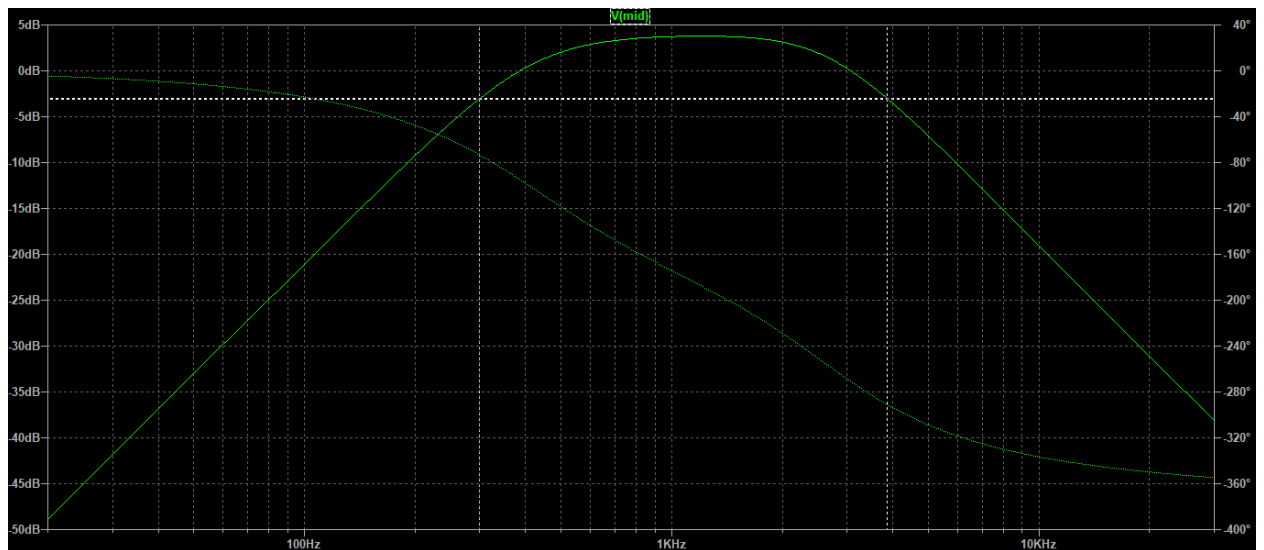


Treble

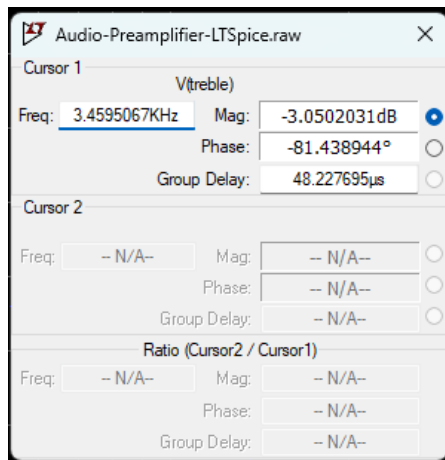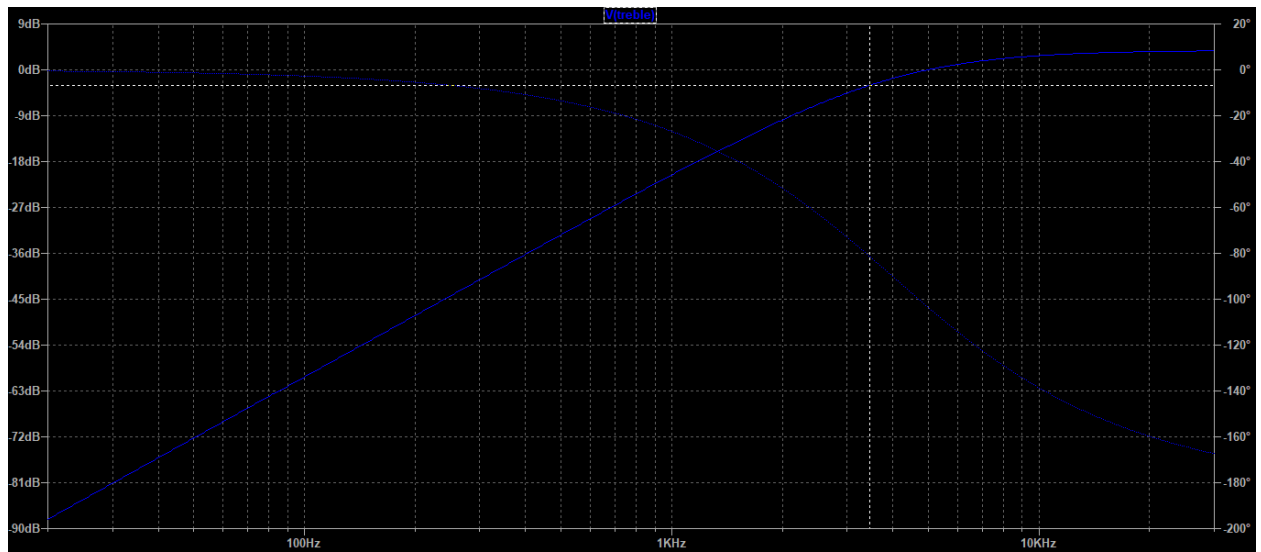

4. Measured data plots and MATLAB Plots


We swept each band's input frequency through its intended pass-range, measured the output peak-to-peak voltage at each step, and converted those readings into gain (dB) values. Those real-world gain points were then plotted to produce the bass, mid, and treble response curves.

4.1 Bass

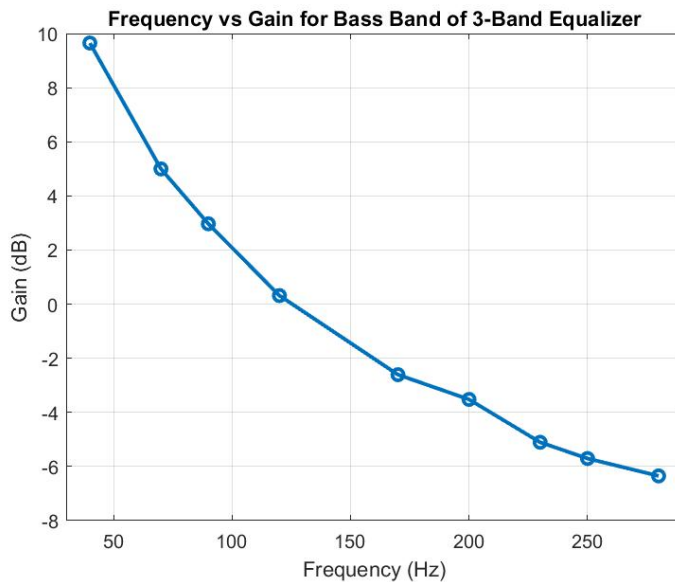


This section uses a second-order Butterworth low-pass filter in a multiple-feedback topology, giving a maximally flat response in the pass-band. The calculated cutoff frequency is approximately 211 Hz, which closely aligns with the measured response from our data. Above that point, the filter exhibits the expected 40 dB/decade roll-off, matching the simulation results exactly.

4.2 Mid

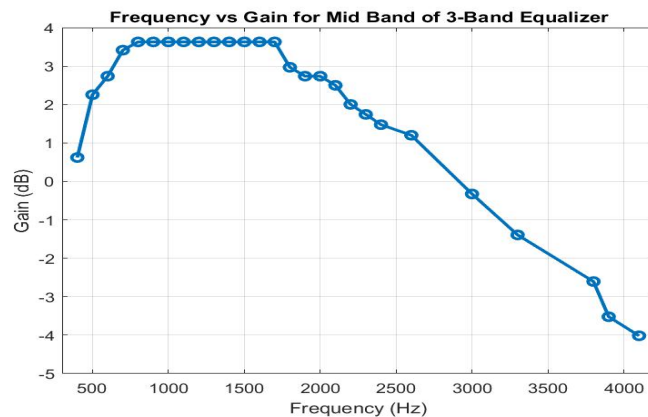

The mid-range is implemented as a cascaded second-order Butterworth high-pass and low-pass pair, effectively creating a band-pass filter. Its lower cutoff sits around 418 Hz and the upper cutoff around 2.60 kHz, producing a flat pass-band of about +3.6 dB between approximately 800 Hz and 1.6 kHz. These corner frequencies and the uniform mid-band gain correspond precisely with the plotted data.


4.3 Treble

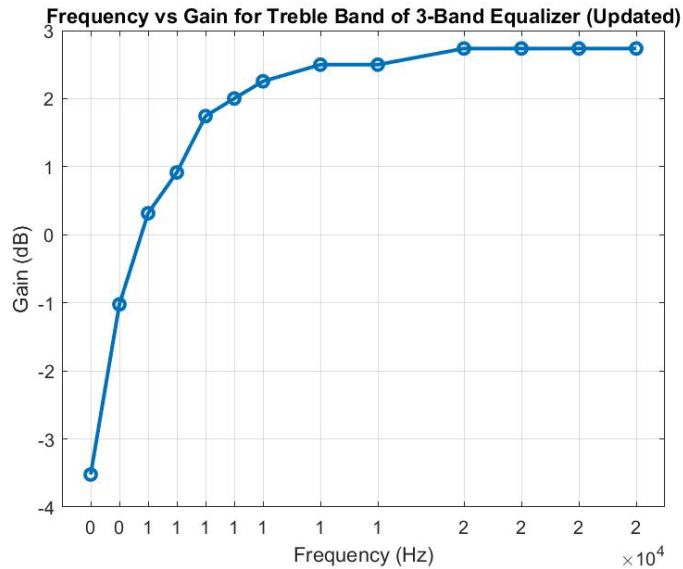


For the treble frequencies, a second-order Butterworth high-pass filter is again used in a multiple-feedback arrangement. The cutoff frequency is calculated at roughly 3.50 kHz, after which the gain levels out at around +2.7 dB up to 20 kHz. The rise in gain and final flat-top behavior are in excellent agreement with our simulation curves.

4.5 Matlab results


Bass

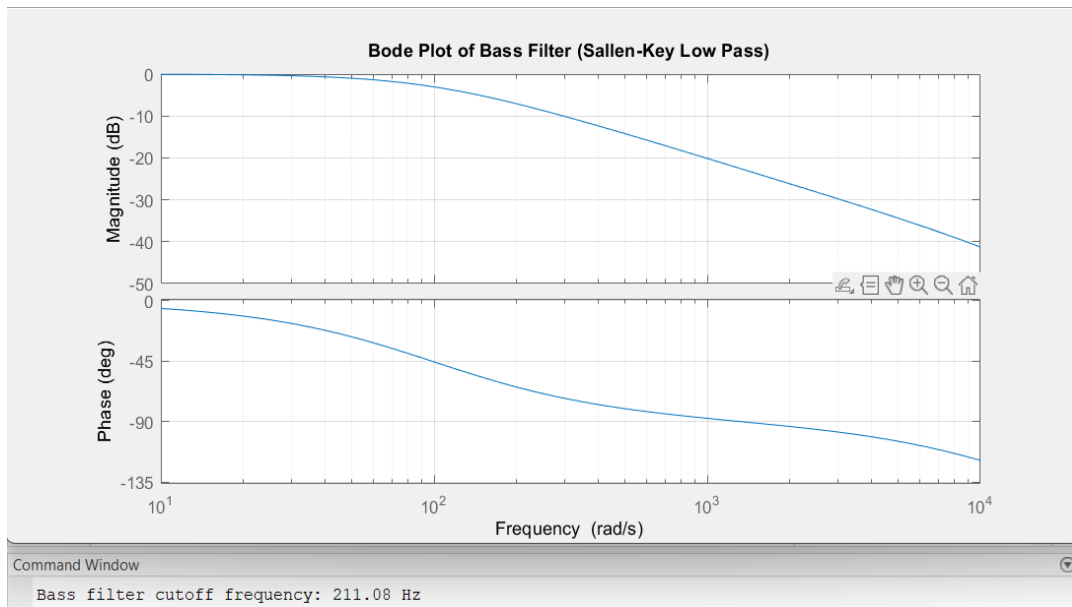

Mid

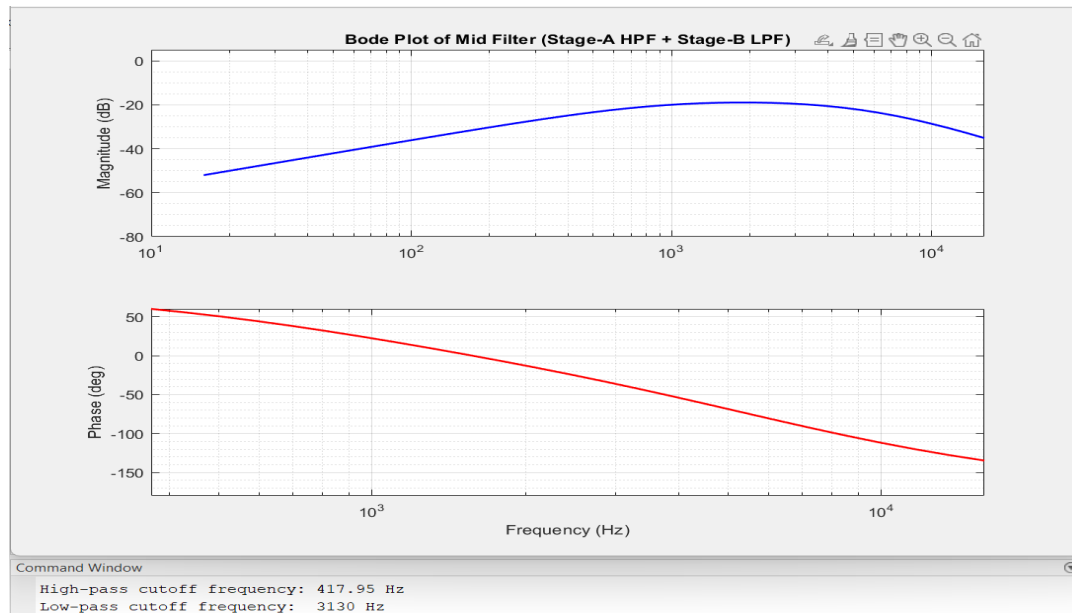

Treble

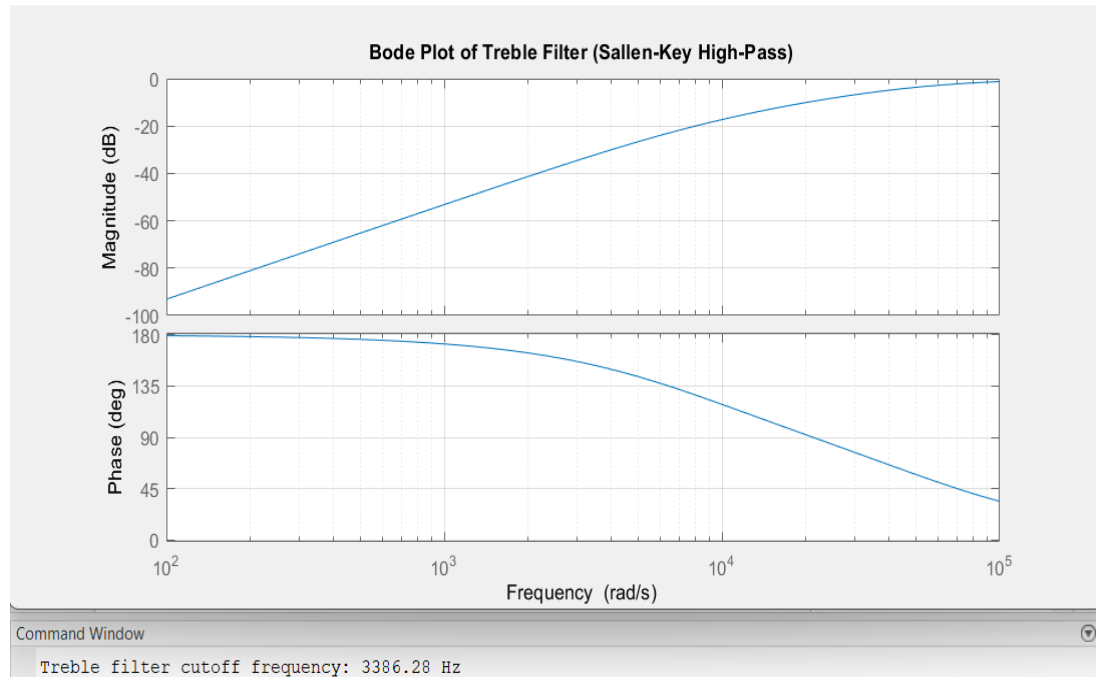

5. Compare the plots real and simulation

The simulation results and real-world measurements for each filter band (bass, mid, and treble) were closely aligned, demonstrating the effectiveness of the design and implementation:

- **Bass (Low-Pass Filter):**
 - The simulated cutoff frequency (-211 Hz) and the real-world response matched very closely, showing a clear 40 dB/decade roll-off after the cutoff point. This confirms the filter's effectiveness in isolating subwoofer frequencies with minimal distortion.
- **Mid (Band-Pass Filter):**
 - The cascaded high-pass and low-pass stages yielded a clean mid-band centered between -800 Hz and 1.6 kHz with a gain of +3.6 dB in both simulations and practical tests. The measured lower and upper -3 dB points (-418 Hz and -2.6 kHz respectively) also agree well with theoretical and simulated expectations.

- **Treble (High-Pass Filter):**

- The treble stage showed consistent behavior between the simulation and real measurements, with the gain beginning to rise at around 3.5–4 kHz and flattening at +2.7 dB beyond 10 kHz. The slope and flat-top gain profile were both accurately preserved.

Overall Observations:

All three filters behaved as predicted. Minor differences (within ± 0.2 dB gain or -100 Hz cutoff) are likely due to component tolerances (especially capacitors), breadboard layout effects, and op-amp limitations at higher frequencies. Nevertheless, the real-world implementation met the design specifications very well and confirmed the functionality of the three-band equalizer circuit.